

Operational Amplifier Building Blocks

Operational Amplifiers are used to amplify signals from DC to tens of megahertz and can do so in a variety of different op-amp configurations


We have seen that we can connect resistors to a basic operational amplifier to produce various inverting and non-inverting outputs and configurations along with their respective gains.

So to make things a little bit easier for all, here is a list of some of the “Basic Operational Amplifier Building Blocks” we can use to create different electronic circuits and filters.

The Voltage Follower

The Voltage Follower, also called a buffer does not amplify or invert the input signal but instead provides isolation between two circuits. The input impedance is very high while the output impedance is low avoiding any loading effects within the circuit. As the output is connected back directly to one of the inputs, the overall gain of the buffer is **+1** and $V_{out} = V_{in}$.


The Voltage Follower Op-amp Circuit

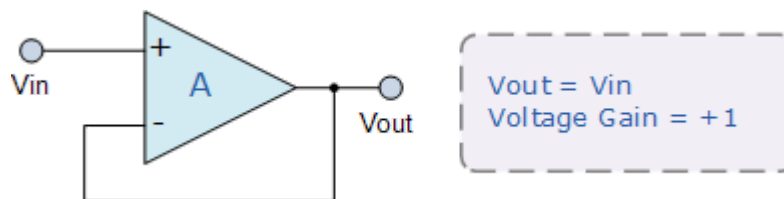

The Op-amp Inverter

The Inverter, also called an inverting buffer is the opposite to that of the previous voltage follower. The inverter does not amplify if both resistances are equal but does invert the input signal. The input impedance is equal to R and the gain is **-1** giving $V_{out} = -V_{in}$.

The Op-amp Inverter Circuit

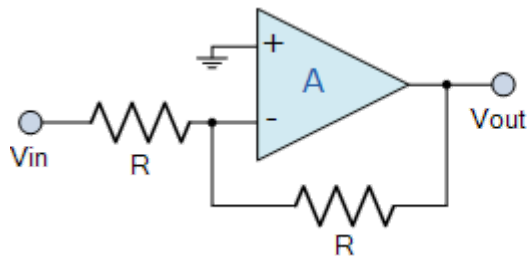


Voltage Gain = -1
Input Impedance = R

The Non-inverting Amplifier

The Non-inverting Amplifier does not invert the input signal or produce an inverting signal but instead amplifies it by the ratio of: $(R_A + R_B)/R_B$ or commonly $1 + (R_A/R_B)$. The input signal is connected to the non-inverting (+) input.

The Non-inverting Op-amp Circuit

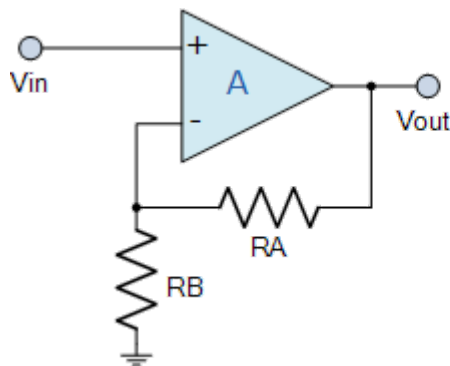


$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_A}{R_B}$$

The Inverting Amplifier

The Inverting Amplifier both inverts and amplifies the input signal by the ratio of $-R_A/R_B$. The gain of the amplifier is controlled by negative feedback using the feedback resistor R_A and the input signal is fed to the inverting (-) input.

The Inverting Op-amp Circuit

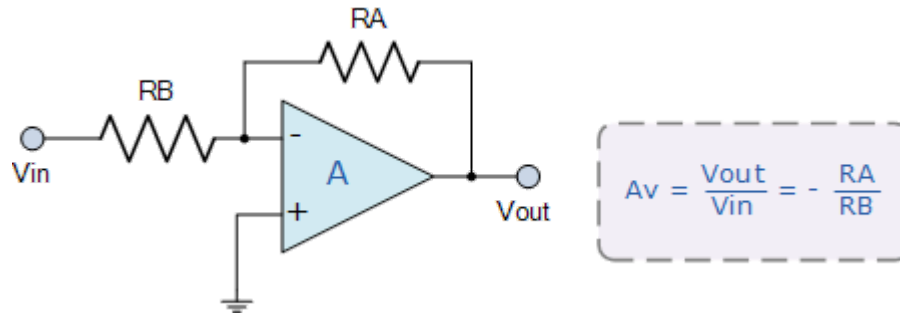


The Bridge Amplifier

The inverting and non-inverting amplifier circuits from above can be connected together to form a bridge amplifier configuration. The input signal is common to both op-amps with the output voltage signal taken across the load resistor, R_L which floats between the two outputs.

If the magnitudes of the two op-amp gains, A_1 and A_2 are equal to each other, then the output signal will be doubled as it is effectively the combination of the two individual amplifier gains.

The Bridge Op-amp Circuit

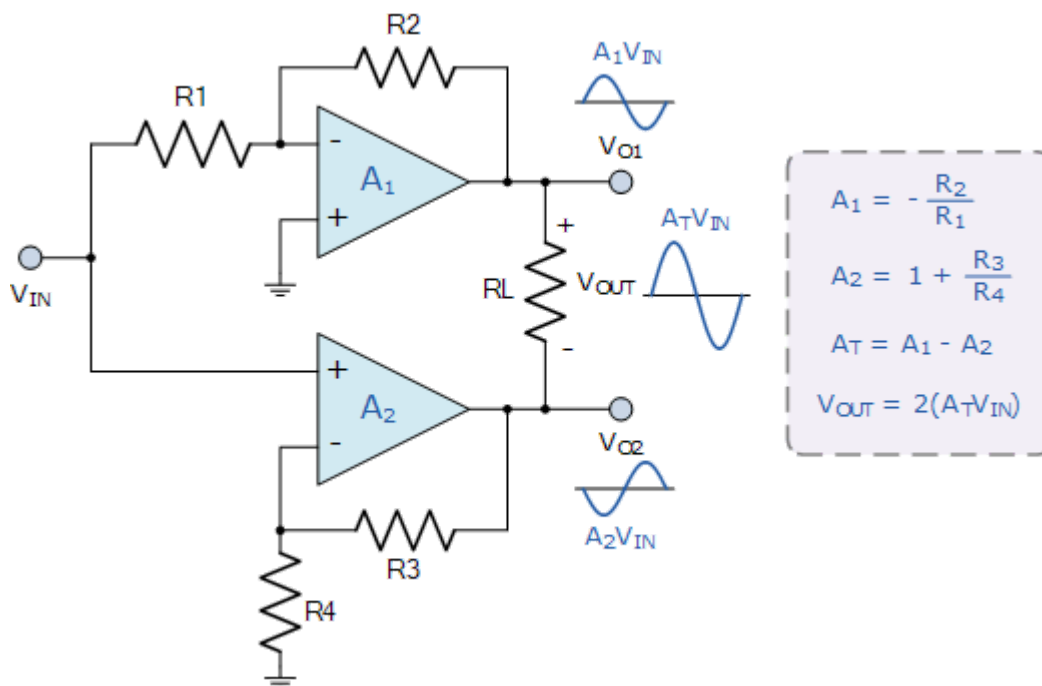


The Voltage Adder

The Adder, also called a summing amplifier, produces an inverted output voltage which is proportional to the sum of the input voltages V_1 and V_2 . More inputs can be summed. If the input resistors are equal in value ($R_1 = R_2 = R$) then the summed output voltage is as given and the gain

is **+1**. If the input resistors are unequal then the output voltage is a weighted sum and becomes:

$$V_{out} = -(V_1(RA/R_1) + V_2(RA/R_2) + \text{etc.})$$

The Voltage Adder Op-amp Circuit

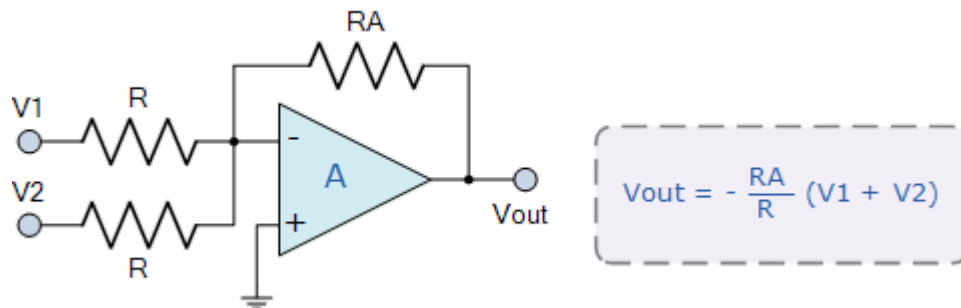


The Voltage Subtractor

The Subtractor also called a differential amplifier, uses both the inverting and non-inverting inputs to produce an output signal which is the difference between the two input voltages V_1 and V_2 allowing one signal to be subtracted from another. More inputs can be added to be subtracted if required.

If resistances are equal ($R = R_3$ and $RA = R_4$) then the output voltage is as given and the voltage gain is **+1**. If the input resistance are unequal the circuit becomes a differential amplifier producing a negative output when V_1 is higher than V_2 and a positive output when V_1 is lower than V_2 .

The Voltage Subtractor Op-amp Circuit

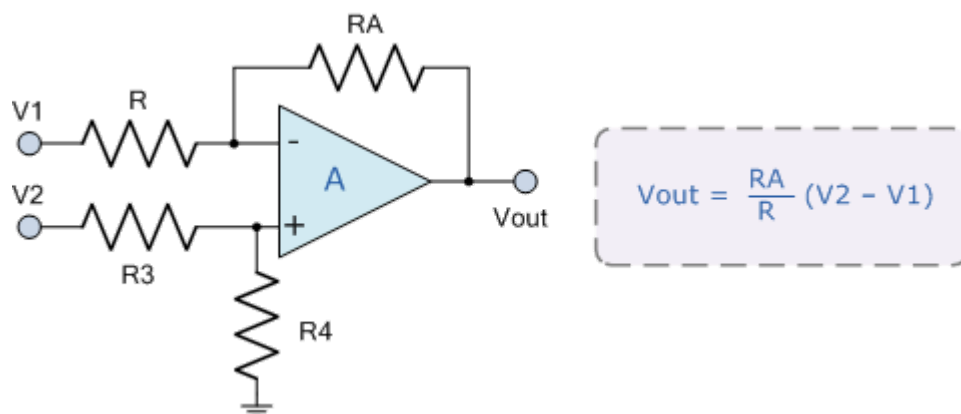


The Op-amp Comparator

The Comparator has many uses but the most common is to compare the input voltage to a reference voltage and switch the output if the input voltage is above the reference voltage. If the input goes more positive than the reference voltage set by the voltage divider, $V_{in} > V_{ref}$, the

output changes state.

When the input voltage drops below the preset reference voltage and $V_{in} < V_{ref}$, the output switches back. By using positive feedback the basic comparator circuit can easily be converted into a Schmitt Trigger to reduce oscillations around the switching point.

The Comparator Op-amp Circuit

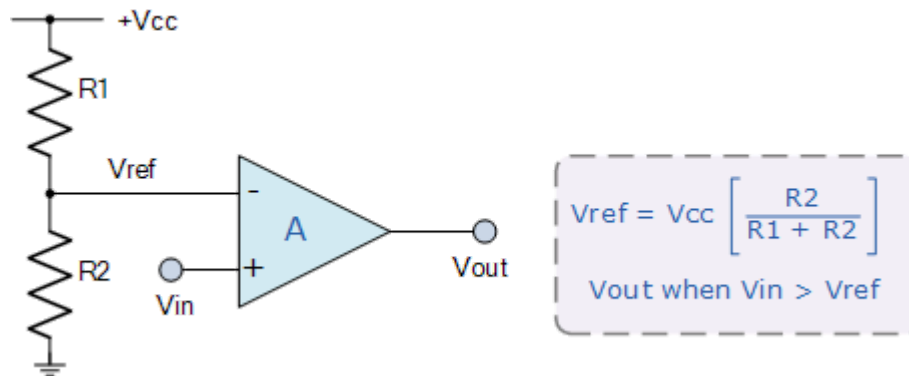

Here are just some of the more common and basic operational amplifier building block configurations discussed in this section that we can use in electronic circuits. All the above circuits can be constructed using a variety of different op-amps including the famous 741 op-amp. I hope that this short tutorial about basic op-amp building blocks will help you to understand the different basic op-amp circuit configurations.