


The RC Oscillator Circuit

RC Oscillators use a combination of an amplifier and an RC feedback network to produce output oscillations due to the phase shift between the stages

In the amplifier tutorials we saw that a single stage transistor amplifier can produce 180° of phase shift between its output and input signals when connected as a common-emitter type amplifier and that its output signal across the collector load depends entirely on the input signal injected into the transistors base terminal.

But we can configure transistor stages to operate as oscillators by placing resistor-capacitor (RC) networks around the transistor to provide the required regenerative feedback without the need for a tank circuit. Frequency selective RC coupled amplifier circuits are easy to build and can be made to oscillate at any desired frequency by selecting the appropriate values of resistance and capacitance.

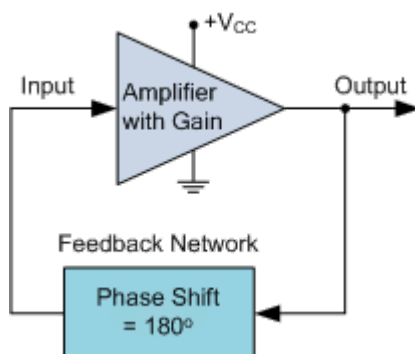
For an RC oscillator to sustain its oscillations indefinitely, sufficient feedback of the correct phase, that is positive (in-phase) Feedback must be provided along with the voltage gain of the single transistor amplifier being used to inject adequate loop gain into the closed-loop circuit in order to maintain oscillations allowing it to oscillates continuously at the selected frequency.



In an **RC Oscillator** circuit the input is shifted 180° through the feedback circuit returning the signal out-of-phase and 180° again through an inverting amplifier stage to produces the required positive feedback. This then gives us " $180^\circ + 180^\circ = 360^\circ$ " of phase shift which is effectively the same as 0° , thereby giving us the required positive feedback. In other words, the total phase shift of the feedback loop should be "0" or any multiple of 360° to obtain the same effect.

In a **Resistance-Capacitance Oscillator** or simply known as an **RC Oscillator**, we can make use of the fact that a phase shift occurs between the input to a RC network and the output from the same network by using interconnected RC elements in the feedback branch, for example.

RC Phase-Shift Network

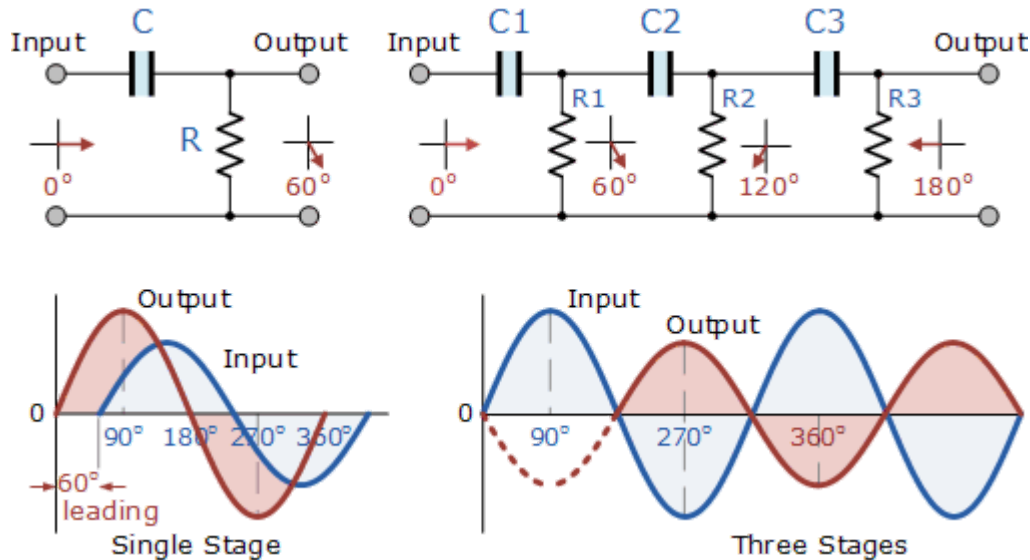

The circuit on the left shows a single resistor-capacitor network whose output voltage “leads” the input voltage by some angle less than 90° . In a pure or ideal single-pole RC network, it would produce a maximum phase shift of exactly 90° , and because 180° of phase shift is required for oscillation, at least two single-poles networks must be used within an *RC oscillator* design.

However in reality it is difficult to obtain exactly 90° of phase shift for each RC stage so we must therefore use more RC stages cascaded together to obtain the required value at the oscillation frequency. The amount of actual phase shift in the circuit depends upon the values of the resistor (R) and the capacitor (C), at the chosen frequency of oscillations with the phase angle (φ) being given as:

RC Phase Angle

$$X_C = \frac{1}{2\pi f C} \quad R = R,$$


$$Z = \sqrt{R^2 + (X_C)^2}$$

$$\therefore \phi = \tan^{-1} \frac{X_C}{R}$$

Where: X_C is the Capacitive Reactance of the capacitor, R is the Resistance of the resistor, and f is the Frequency.


In our simple example above, the values of R and C have been chosen so that at the required frequency the output voltage leads the input voltage by an angle of about 60° . Then the phase angle between each successive RC section increases by another 60° giving a phase difference between the input and output of 180° ($3 \times 60^\circ$) as shown by the following vector diagram.

Vector Diagram

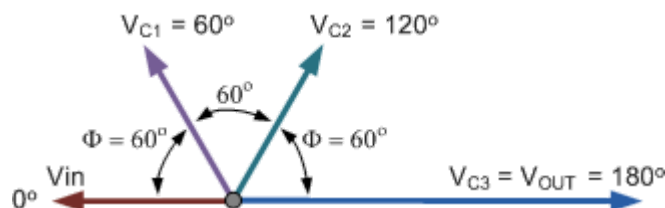


So by cascading together three such RC networks in series we can produce a total phase shift in the circuit of 180° at the chosen frequency and this forms the bases of a "RC Oscillator" otherwise known as a **Phase Shift Oscillator** as the phase angle is shifted by an amount through each stage of the circuit. Then the phase shift occurs in the phase difference between the individual RC stages. Conveniently op-amp circuits are available in quad IC packages. For example, the LM124, or the LM324, etc. so four RC stages could also be used to produce the required 180° of phase shift at the required oscillation frequency.

We know that in an amplifier circuit either using a Bipolar Transistor or an Inverting Operational Amplifier configuration, it will produce a phase-shift of 180° between its input and output. If a three-stage RC phase-shift network is connected as a feedback network between the output and input of an amplifier circuit, then the total phase shift created to produce the required regenerative feedback is: $3 \times 60^\circ + 180^\circ = 360^\circ = 0^\circ$ as shown.

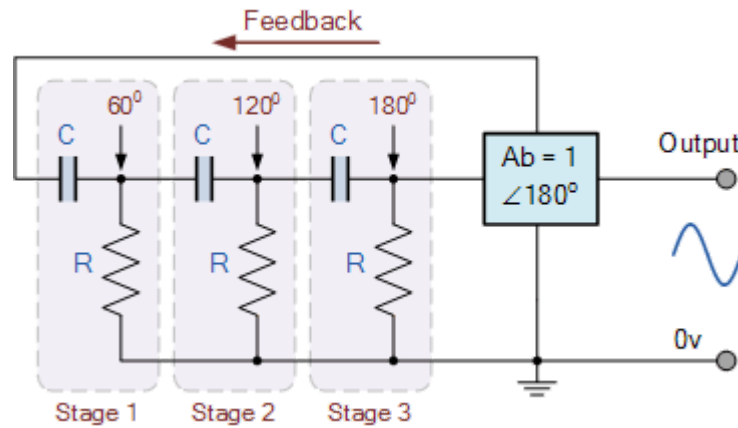

The three RC stages are cascaded together to obtain the required slope for a stable oscillation frequency. The feedback loop phase shift is -180° when the phase shift of each stage is -60° . This occurs when $\omega = 2\pi f = 1.732/RC$ as ($\tan 60^\circ = 1.732$). Then to achieve the required phase shift in an RC oscillator circuit is to use multiple RC phase-shifting networks such as the circuit below.

Basic RC Oscillator Circuit

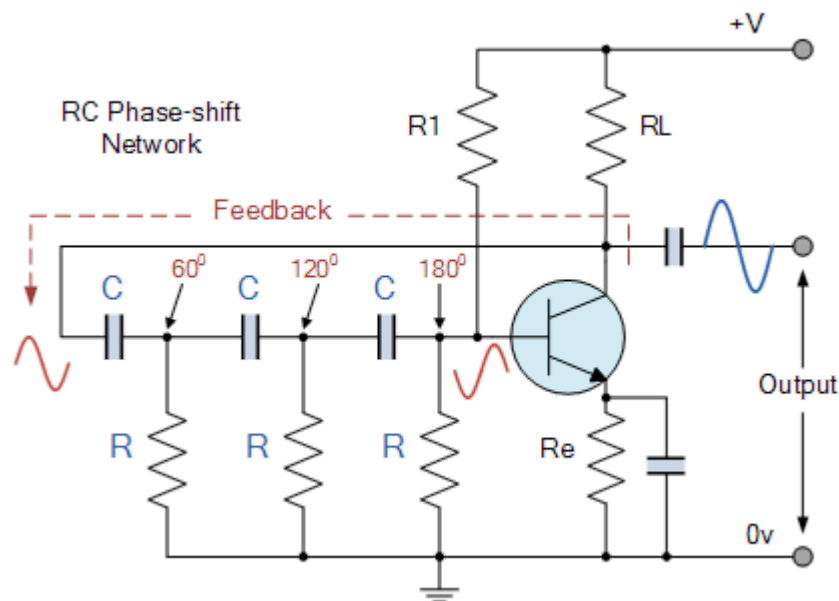

The basic **RC Oscillator** which is also known as a **Phase-shift Oscillator**, produces a sine wave output signal using regenerative feedback obtained from the resistor-capacitor (RC) ladder network. This regenerative feedback from the RC network is due to the ability of the capacitor to store an electric charge, (similar to the LC tank circuit).

This resistor-capacitor feedback network can be connected as shown above to produce a leading phase shift (phase advance network) or interchanged to produce a lagging phase shift (phase retard network) the outcome is still the same as the sine wave oscillations only occur at the frequency at which the overall phase-shift is 360° .

By varying one or more of the resistors or capacitors in the phase-shift network, the frequency can be varied and generally this is done by keeping the resistors the same and using a 3-ganged variable capacitor because capacitive reactance (X_C) changes with a change in frequency as capacitors are frequency-sensitive components. However, it may be required to re-adjust the voltage gain of the amplifier for the new frequency.

If the three resistors, R are equal in value, that is $R_1 = R_2 = R_3$, and the capacitors, C in the phase shift network are also equal in value, $C_1 = C_2 = C_3$, then the frequency of oscillations produced by the RC oscillator is simply given as:

$$f_r = \frac{1}{2\pi RC\sqrt{2N}}$$

Where:

f_r is the oscillators output frequency in Hertz

R is the feedback resistance in Ohms

C is the feedback capacitance in Farads

N is the number of RC feedback stages.

This is the frequency at which the phase shift circuit oscillates. In our simple example above, the number of stages is given as three, so $N = 3$ ($\sqrt{2*3} = \sqrt{6}$). For a four stage RC network, $N = 4$ ($\sqrt{2*4} = \sqrt{8}$), etc.


Since the resistor-capacitor combination in the **RC Oscillator** ladder network also acts as an attenuator, that is the signal reduces by some amount as it passes through each passive stage. It could be assumed that the three phase shift sections are independent of each other but this is not the case as the total accumulative feedback attenuation becomes $-1/29$ th ($V_o/V_i = \beta = -1/29$) across all three stages. Thus the voltage gain of the amplifier must be sufficiently high enough to overcome these passive RC losses. Clearly then in order to produce a total loop gain of -1 , in our three stage RC network above, the amplifier gain must be equal too, or greater than, 29 to compensate for the attenuation of the RC network.

The loading effect of the amplifier on the feedback network has an effect on the frequency of oscillations and can cause the oscillator frequency to be up to 25% higher than calculated. Then the feedback network should be driven from a high impedance output source and fed into a low impedance load such as a common emitter transistor amplifier but better still is to use an **Operational Amplifier** as it satisfies these conditions perfectly.

The Op-amp RC Oscillator

When used as RC oscillators, **Operational Amplifier RC Oscillators** are more common than their bipolar transistors counterparts. The oscillator circuit consists of a negative-gain operational amplifier and a three section RC network that produces the 180° phase shift. The phase shift network is connected from the op-amps output back to its "inverting" input as shown below.


Op-amp Phase-lead RC Oscillator Circuit

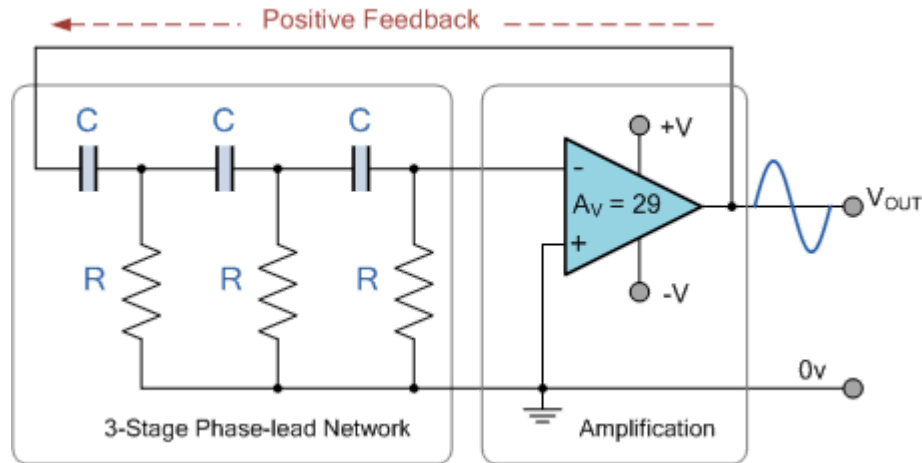

As the feedback is connected to the inverting input, the operational amplifier is therefore connected in its “inverting amplifier” configuration which produces the required 180° phase shift while the RC network produces the other 180° phase shift at the required frequency ($180^\circ + 180^\circ$). This type of feedback connection with the capacitors in series and the resistors connected to ground (0V) potential is known as a *phase-lead* configuration. In other words, the output voltage leads the input voltage producing a positive phase angle.

But we can also create a *phase-lag* configuration by simply changing the positions of the RC components so that the resistors are connected in series and the capacitors are connected to ground (0V) potential as shown. This means that the output voltage lags the input voltage producing a negative phase angle.

Op-amp Phase-lag RC Oscillator Circuit

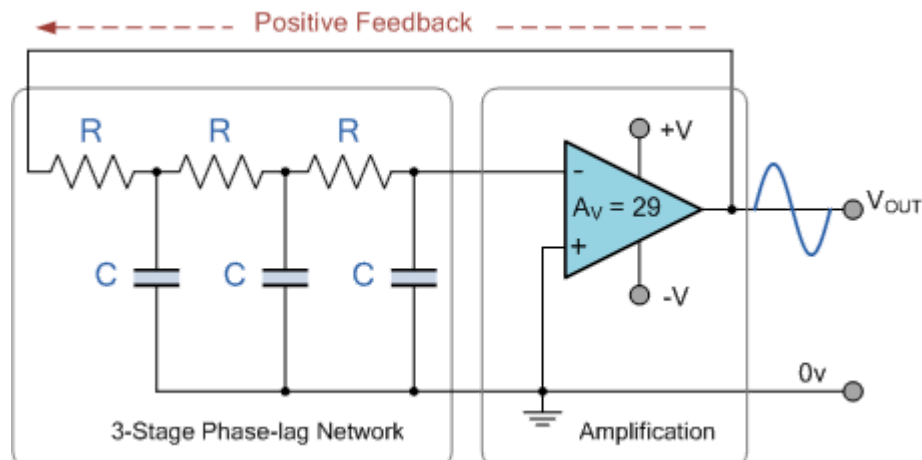

However, due to the reversal of the feedback components, the original equation for the frequency output of the phase-lead RC oscillator is modified to:

$$f_r = \frac{\sqrt{2N}}{2\pi RC}$$

Although it is possible to cascade together only two single-pole RC stages to provide the required 180° of phase shift (90° + 90°), the stability of the oscillator at low frequencies is generally poor.

One of the most important features of an **RC Oscillator** is its frequency stability which is its ability to provide a constant frequency sine wave output under varying load conditions. By cascading three or even four RC stages together (4 x 45°), the stability of the oscillator can be greatly improved.

RC Oscillators with four stages are generally used because commonly available operational amplifiers come in quad IC packages so designing a 4-stage oscillator with 45° of phase shift relative to each other is relatively easy.

RC Oscillators are stable and provide a well-shaped sine wave output with the frequency being proportional to 1/RC and therefore, a wider frequency range is possible when using a variable capacitor. However, RC Oscillators are restricted to frequency applications because of their bandwidth limitations to produce the desired phase shift at high frequencies.

RC Oscillator Example No1

An operational amplifier based *3-stage RC Phase Shift Oscillator* is required to produce a sinusoidal output frequency of 4kHz. If 2.4nF capacitors are used in the feedback circuit, calculate the value of the frequency determining resistors and the value of the feedback resistor required to sustain oscillations. Also draw the circuit.

The standard equation given for the phase shift RC Oscillator is:

$$f_r = \frac{1}{2\pi RC\sqrt{2N}}$$

The circuit is to be a 3-stage RC oscillator which will therefore consist of equal resistors and three equal 2.4nF capacitors. As the frequency of oscillation is given as 4.0kHz, the value of the resistors are calculated as:

$$f = 4.0\text{kHz} = \frac{1}{2\pi\sqrt{(2 \times 3)} \times R \times 2.4\text{nF}}$$

$$R = \frac{1}{2\pi\sqrt{(6)} \times 4000 \times 2.4 \times 10^{-9}}$$


$$\therefore R = 6770\Omega \text{ or } 6.8\text{k}\Omega$$

The operational amplifiers gain must be equal to 29 in order to sustain oscillations. The resistive value of the oscillation resistors are 6.8k Ω , therefore the value of the op-amps feedback resistor R_f is calculated as:

$$A_V = \frac{R_F}{R} = 29$$

$$\therefore R_F = A_V \times R = 29 \times 6.8\text{k}\Omega = 197.2\text{k}\Omega$$

RC Oscillator Op-amp Circuit

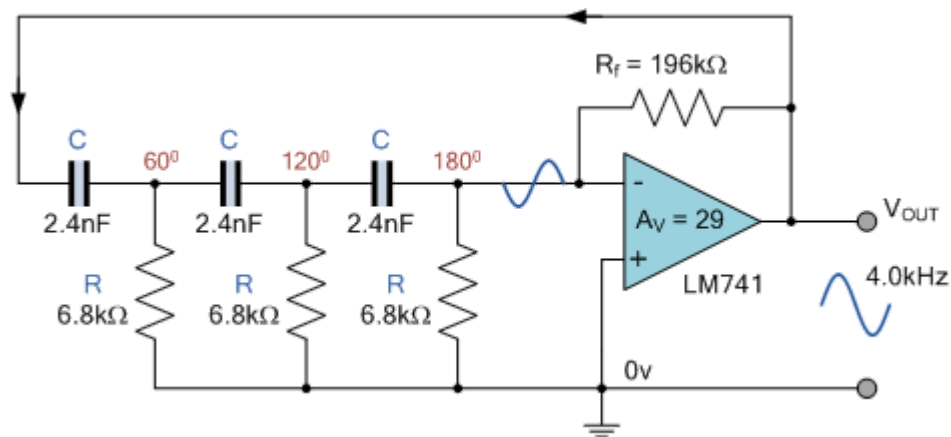

In the next tutorial about Oscillators, we will look at another type of **RC Oscillator** called a Wien Bridge Oscillators which uses resistors and capacitors as its tank circuit to produce a low frequency sinusoidal waveform.